

# Multivibrators


## 1. Introduction

### *Types of multivibrators*

Multivibrator circuits are positive feedback universal digital circuits used to generate square waves. Their output voltage does not change continuously but can take on two discrete values. The flip can occur in several different ways. Accordingly, there are:

- bistable multivibrator --- both states are stable. The output signal level only changes when the switching process is triggered by an input signal.
- monostable multivibrator --- has one stable state. Its unstable state can be triggered by an input signal and lasts only for a period of time determined by the values of the components. After this time has elapsed, the circuit automatically returns to its stable state.
- astable multivibrator --- has no stable state. Without external control, it periodically changes its output voltage level, oscillating between its two states.

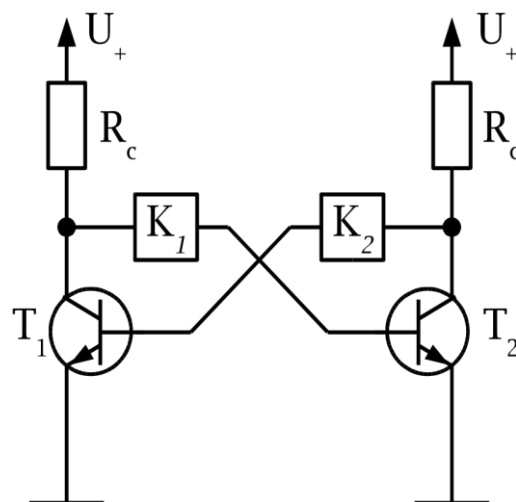Oscillating circuits are generally shown in Figure 1. The type of oscillating circuit is determined by the feedback loop ( $K_1$ ,  $K_2$ ) (Table 1).




1. Figure--Block scheme of a multivibrators

Type	$K_1$	$K_2$
Bistable	R	R
Monostable	R	C
Astable	C	C

1. table--Feedback loops of multivibrators
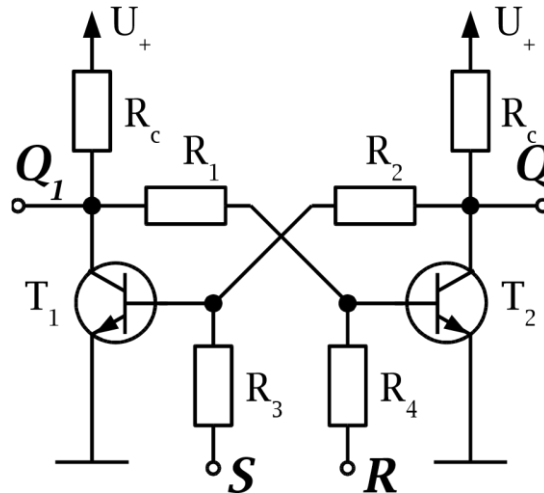
## 2. Bistable multivibrator (flip-flop)

The circuit implementation of the bistable flip-flop is shown in Figure 2.



**2. Figure–Bistable multivibrator**


In the default state, no signal is applied to either the S or R input. In this case, the circuit is in one of the two stable states and remains there (either  $Q_1=0V$  and  $Q_2=U_+$ , or  $Q_1=U_+$  and  $Q_2=0V$ , where  $U_+$  denotes the supply voltage). Let us assume that our circuit is in the latter state. If we apply supply voltage to the S input, the transistor opens due to the current flowing through the  $T_1$  emitter-base diode, and the  $T_1$  collector voltage decreases. As a result, the  $T_2$  base current decreases and the  $T_2$  collector voltage increases. This increase feeds back through resistor  $R_2$  to the base of  $T_1$  and further increases its base current (positive feedback).

The circuit reaches a stable state when  $T_1$  is fully open.  $T_2$  is then fully closed and keeps  $T_1$  open via  $R_2$ . After this, we can disconnect the supply voltage from the S input, and the circuit remains in a stable state.

We can cause the circuit to switch to another stable state by applying supply voltage to the R input. If power is applied to both inputs simultaneously, both transistors will open. This state is unstable. If we then remove the voltage from the inputs, the asymmetry of the circuit elements will determine which stable state the circuit will switch to. Since the final state cannot be clearly determined in this case, this input combination must be excluded. If we ensure this, then the two outputs ( $Q_1$ ,  $Q_2$ ) of the bistable multivibrator (flip-flop) are logically negated with respect to each other.

This circuit is a **memory element**, as it "remembers" the last state it was set to. It can be set with a signal applied to the S input (set) and reset with a signal applied to the R input (reset). Old static RAMs were composed of such elements.

### 3. Monostable multivibrator

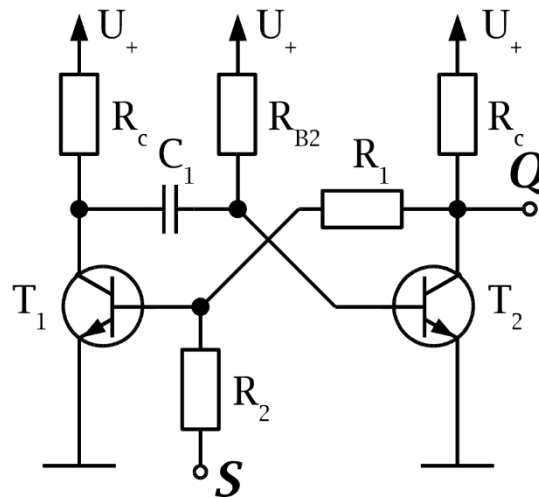

**3. Figure–Monostable multivibrator**

The circuit solution for a monostable multivibrator can be based on a flip-flop circuit. One of the feedback resistors is replaced with a capacitor. The DC operating point of  $T_2$  must be set with a resistor. This circuit is shown in Figure 3.

Let's assume that  $T_1$  is in a closed state and the  $T_2$  transistor is conducting (base current flows through  $R_{B2}$ ). This is the stable state of the circuit. A short positive input pulse applied to  $S$  opens  $T_1$ , causing the collector voltage of  $T_1$  to drop to nearly zero. This voltage jump is transferred by capacitor  $C_1$  to the base of  $T_2$ , causing  $T_2$  to turn off and its collector voltage rise to the supply voltage. As a result,  $T_1$  remains open via feedback resistor  $R_1$  even if the signal on  $S$  has disappeared. This is not a stable state because the  $C_1$  capacitor begins to charge through the  $R_{B2}$  resistor, causing the base voltage of  $T_2$  to increase. After a time determined by the time constant of the  $R_{B2}C_1$  element,  $T_2$  opens and its collector voltage decreases.  $T_1$  closes and the circuit returns to its stable state. The duration of the output pulse is determined by the time constant of the  $R_C C_1$  element.


#### 3.1. Monostable multivibrator with operational amplifier

The operational amplifier amplifies the difference between the two voltages applied to its inputs:  
 $U_{out} = A(U_1 - U_2)$ .

Operational amplifiers typically have high gain, so they only operate linearly with small voltage differences ( $U_1 - U_2$ ). Larger voltage differences cause them to saturate (the positive or negative supply voltage appears at their output).

The ideal operational amplifier is characterized by the following parameters:

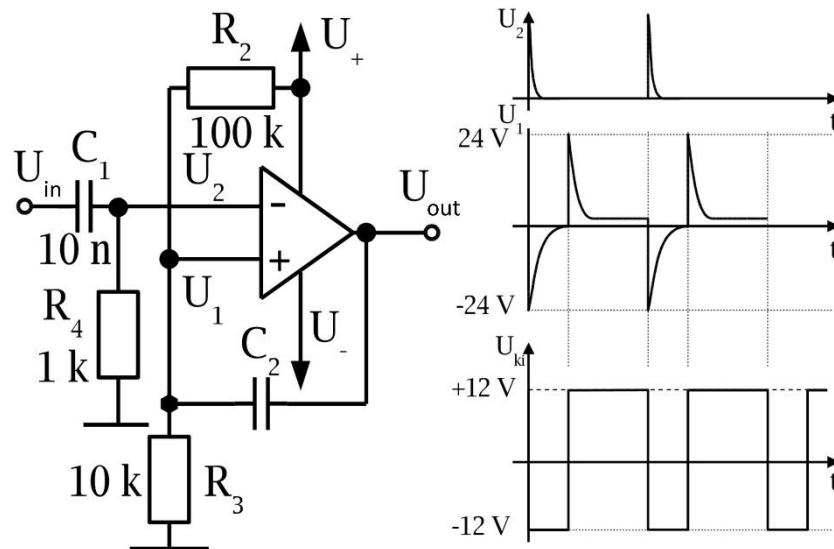- their gain is infinite  $A = \infty$
- their input resistance is infinite  $R_{in} = \infty \Omega$
- their output resistance is zero  $R_{out} = 0 \Omega$



4. Figure – Monostable multivibrator with operational amplifier

If no signal is applied to the input of  $U_{in}$  in the circuit shown in Figure 4 (where  $U_+ = 12V$  and  $U_- = 12V$ ), the inverting input (-) of the amplifier is at ground potential (0V), and the non-inverting input (+) is at a voltage of 1.09V based on the  $R_2$ - $R_3$  voltage divider. The difference between the two inputs causes the amplifier to saturate, resulting in a stable output of +12V.

If we apply a (positive) voltage jump to the  $U_{in}$  input, the  $C_1$  capacitor will allow the voltage change to pass through, causing  $U_2$  to also become positive. If the amplitude of this signal is greater than the potential of the non-inverting input ( $U_1 = 1.09V$ ), the amplifier output level will drop to -12V.

This causes a sudden 24V voltage drop on one plate of the  $C_2$  capacitor.  $C_2$  passes the voltage change, so the 24V voltage drop also appears on its other plate. After the shift, the voltage  $U_1 = -22.91V$  formed at the non-inverting (+) input of the amplifier is not stable, as the  $C_2$  capacitor begins to charge and the voltage at the  $R_3$ - $C_2$  point begins to increase towards the equilibrium 1.09V set by the voltage divider.

When  $U_1$  reaches the voltage level of  $U_2$  (which will return to 0V after the spike appears on it), the circuit returns to its stable state. The return is aided by the capacitor as positive feedback.

According to Thevenin's theorem, the voltage divider can be replaced by a 1.09 V voltage generator with an internal resistance equal to the parallel sum of the resistances of the voltage divider ( $R_p$ ). The current generated in this circuit charges the capacitor. The voltage measured across the capacitor during charging is:


$$U_{C2} = 1,09 \cdot (1 - e^{-\frac{t}{R_p \cdot C_2}}) - 22,91 \cdot e^{-\frac{t}{R_p \cdot C_2}}$$

Expressing the equation in terms of  $t$  and solving it, the time of tipping is:

$$t = R_p C_2 \cdot \ln\left(\frac{24}{1,09}\right)$$
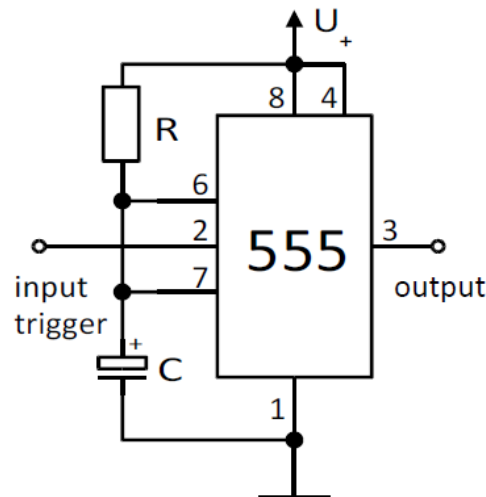
### 3.2. Monostable multivibrator circuit with universal timer 555

In practice, monostable multivibrators are often implemented using an integrated circuit (IC) designed specifically for this purpose: the 555 universal timer. This component can be used to implement timing functions ranging from  $\mu\text{s}$  to several hours.




5. Figure - Monostable multivibrator circuit with universal timer 555

The period time of the IC monostable multivibrator (Figure 5) can be calculated using the following formula:

$$T = 1.1 \cdot R \cdot C [\text{s}]$$
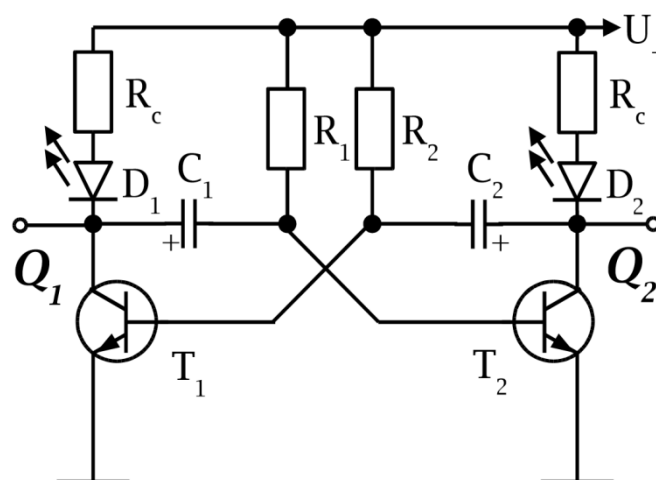
### 4. Astable multivibrator

Multivibrators, as two-state electronic circuits, are suitable for generating square wave signals. A typical astable multivibrator circuit is shown in Figure 6. The role of the light-emitting diodes (LEDs)  $D_1$  and  $D_2$  in the transistor collector circuit is to aid in the visual inspection of voltages.



6. Figure– Astable multivibrator with transistors



Let us assume that the two transistors and the other components form a symmetrical circuit. In this case, both transistors conduct when the circuit is in equilibrium. However, our circuit is not perfectly noise-free.

For example, the switching process causes significant transients. Due to positive feedback through the capacitors (since we feed the signal from  $Q_1$ , which is the output, to the base of the other transistor, which is the input), the circuit is not stable against noise.

Let's assume that due to interference, the collector current of transistor  $T_1$  begins to increase, resulting in an increase in the voltage drop across the resistance  $T_1 R_c$ . This voltage change passes through capacitor  $C_1$ , causing a decrease in the base voltage of  $T_2$ . The  $T_2$  transistor will therefore be less open, i.e., its collector current will decrease, and its collector voltage will increase. This voltage increase passes through the  $C_2$  capacitor, opening the  $T_1$  transistor more, and the process continues until  $T_2$  closes completely. As a result,  $Q_1$  is close to 0V,  $Q_2 = U_+$ , and the LED ( $D_1$ ) lights up.

After a rapid transition due to positive feedback, the capacitors ( $C_1$ - $C_2$ ) begin to charge. The point connected to the collector of  $C_1$  is close to 0V, but the other point is connected to  $U_+$  via resistor  $R_1$ . Therefore, capacitor  $C_1$  begins to charge at a rate determined by the  $R_1 C_1$  time constant. Due to the charging, the voltage at the base of transistor  $T_2$  will reach the opening voltage of the base-emitter diode, and  $T_2$  will begin to open. At this point, a process very similar to the previous one begins, only now on transistor  $T_2$ . Thus, the system switches to its other state, with  $T_2$  open and  $T_1$  closed. At this point,  $Q_2$  is close to 0V, while  $Q_1 = U_+$  and  $D_1$  is not lit.

From the above, the duration of the transitions between the two states is proportional to the charging and discharging times of the capacitors. This time can be controlled by the resistors  $R_1$  and  $R_2$  and the capacitors  $C_1$  and  $C_2$ .  $\tau_1 = R_1 C_1$  and  $\tau_2 = R_2 C_2$ . If  $\tau_1 = \tau_2$ , we obtain a symmetrical square wave. If this is not the case, the two states of the multivibrator have different time constants and the output square wave will also be asymmetrical.



#### 4.1. Astable multivibrator with universal timer 555

This circuit can also be implemented (Figure 7) with a 555 universal timer IC.


The frequency of the square wave can be calculated using the following formula:

$$f = \frac{1}{t_1 + t_2} = \frac{1}{0.693 * C (R_1 + 2R_2)}$$


$$t_1 = 0.693 * C * (R_1 + R_2)$$

$$t_2 = 0.693 * R_2 * C \quad D = \frac{t_1}{t_1 + t_2} = \frac{R_1 + R_2}{R_1 + 2R_2}$$

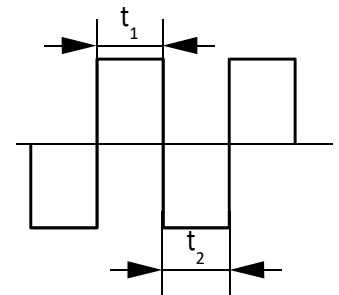$t_1$  and  $t_2$  are the lengths of the periods,  $D$  is the fill factor (the ratio of positive to negative periods).



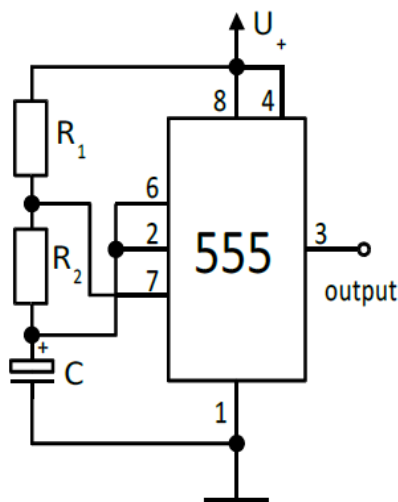7. Figure–Rectangular wave with  $t_1$  and  $t_2$  time periods



8. Figure - Astable multivibrator with universal timer 555









M2: Assemble a monostable multivibrator circuit based on the connection shown in Figure 4 on a breadboard. The duration of the switch (during which the output remains at a low level) should be 200  $\mu$ s. The circuit requires a symmetrical supply voltage ( $\pm 12$ V)! Use a  $\mu$ A741 or TL071 as the operational amplifier (Figure 11).

- Connect the input signal from the function generator to the oscilloscope using a T-splitter and BNC cable. Apply the input signal (100 Hz square wave with a peak value of 5 V) to the circuit using the oscilloscope probe.
- Change the frequency of the input signal first to 500 Hz, then to 1 kHz, and measure the switch time of the circuit.
- In your measurement report, explain why the circuit does not maintain a settling time of nearly 200  $\mu$ s above a certain frequency.
- Take a photo of the circuit and the signal shape displayed on the oscilloscope and include it in your measurement report.

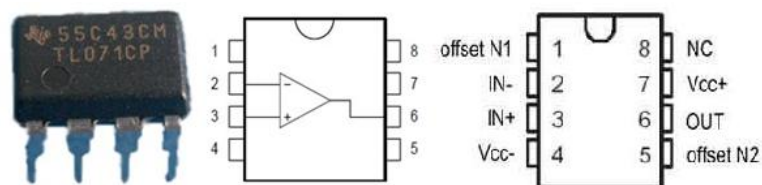

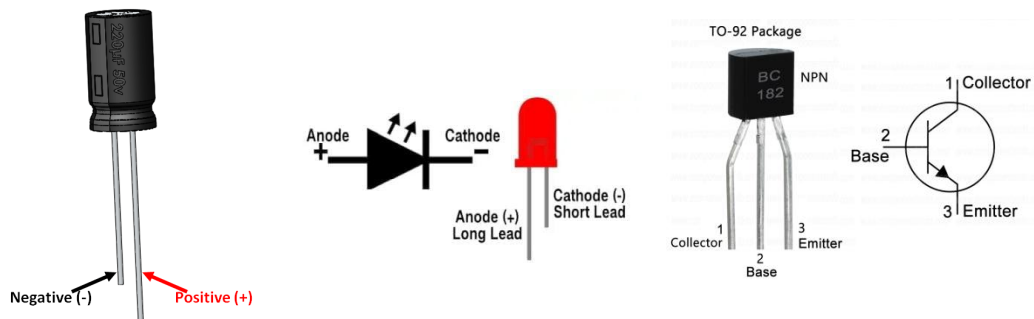11. Figure–Pin assignment of TL071 and  $\mu$ A741



12. Figure – Electrolytic capacitor, LED and transistor connection, pin assignment

The measurement report shall list the measuring instruments, generators, cables, and components used, including their type, model number, quantity, and value, if these can be found on the devices. The size of the photos should be such that the report does not exceed 10 MB. The report should be in the following format: M5\_lastname1\_lastname2.pdf